
Interfacing Diagram:

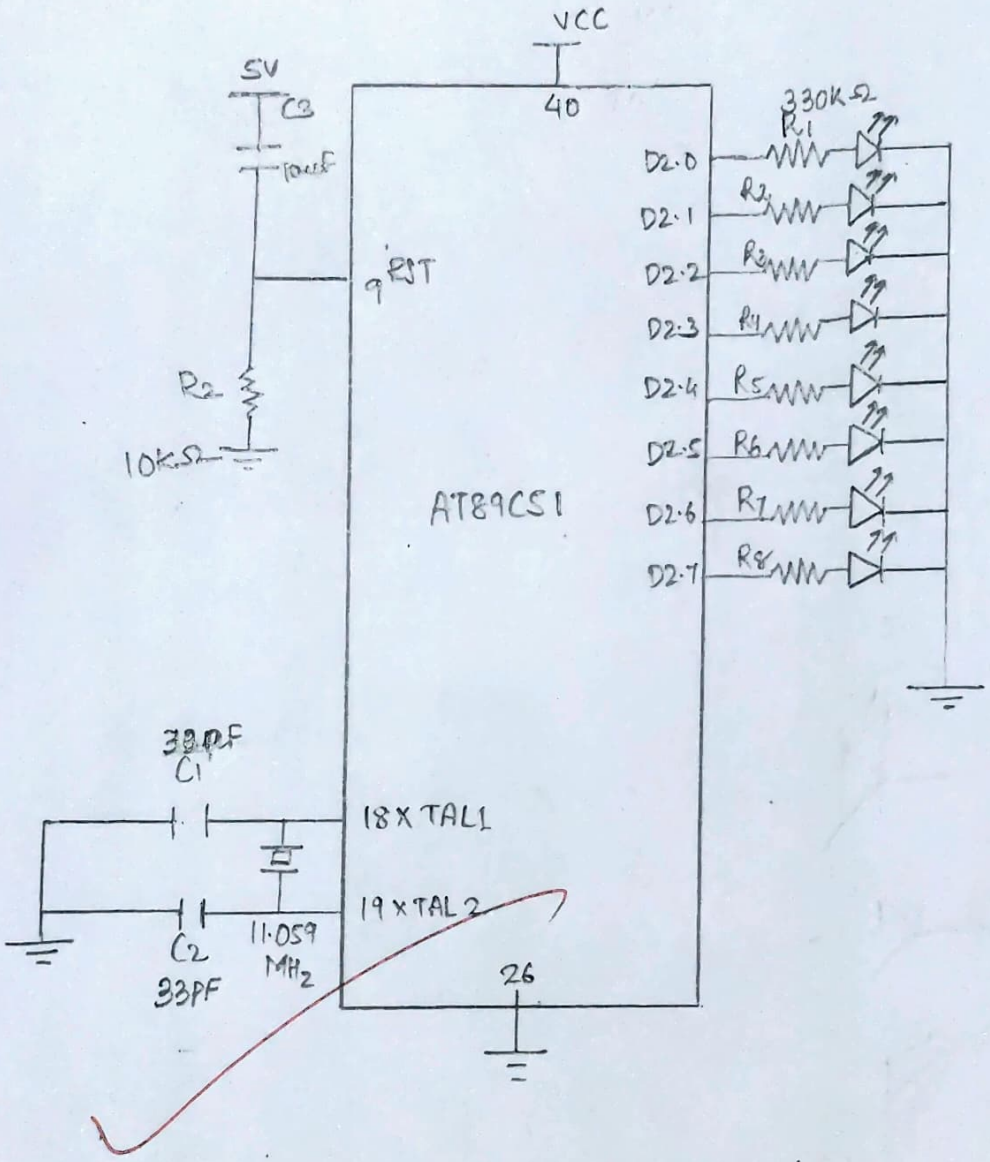Draw an interfacing diagram of LED connected to port 2 with 8051 microcontrollers.




Conclusion:

Thus LED interfacing with 8051 microcontroller was successfully performed. Difference in LED operations such as flashing, binary counting, BCD counting & hexadecimal counting were implemented using Embedded C.

SRM

Interfacing Diagram:

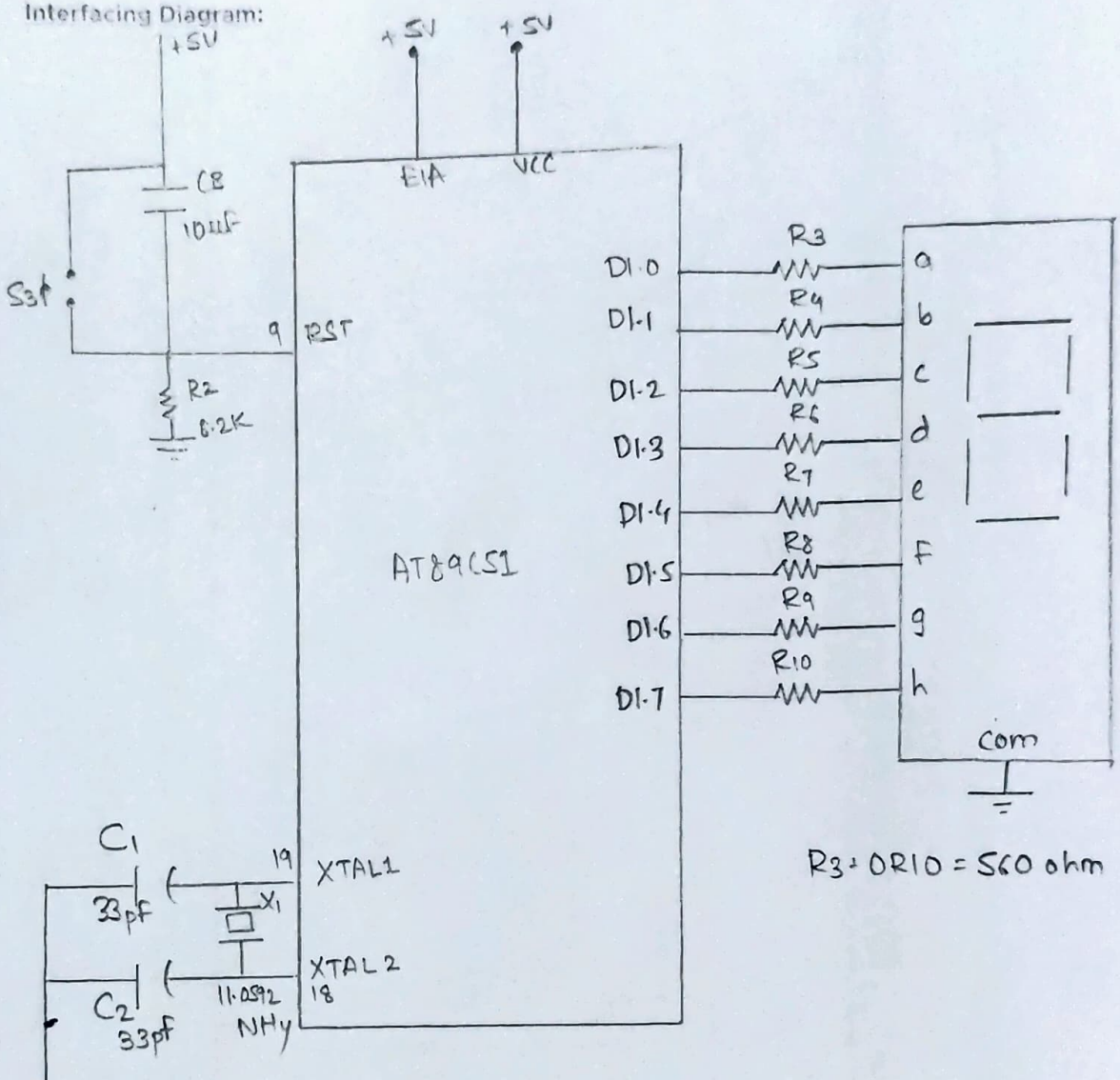

R3 = OR10 = 560 ohm


Conclusion

Thus, the multiplexed seven segment display was successfully interfaced with 8051 microcontroller. Decimal counting was displayed & concept of multiplexing & persistence of vision was understood.

V. Good

Sprinth

Interfacing Diagram:

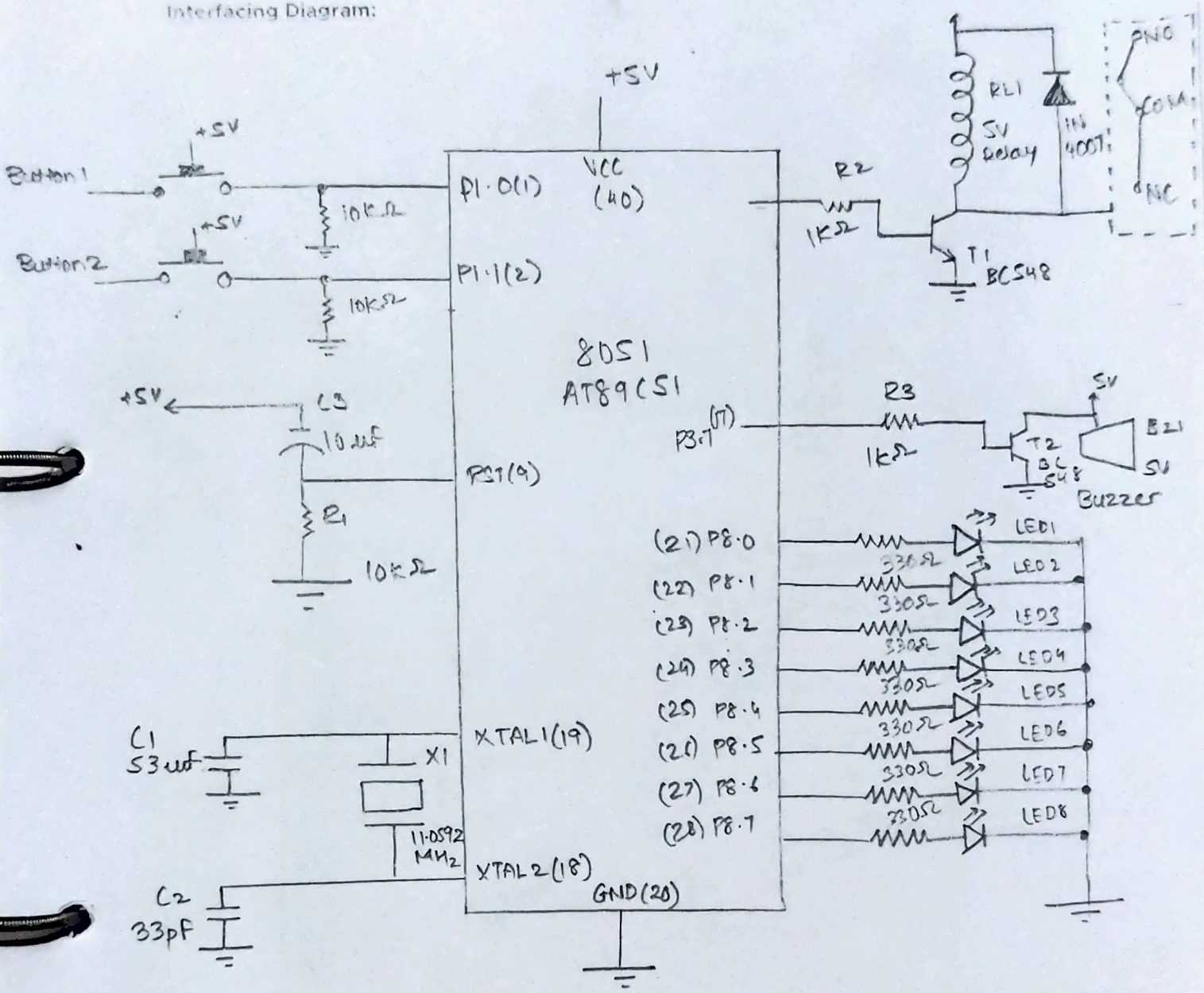


V. good

Conclusion

Thus, push button, relay, buzzer & LEDs were successfully interfaced with 8051 microcontroller. Button 1 activated relay & Buzzer with LED chasing from left to right, while Button 2 deactivated them with LED chasing from right to left.

Superb

Interfacing Diagram:

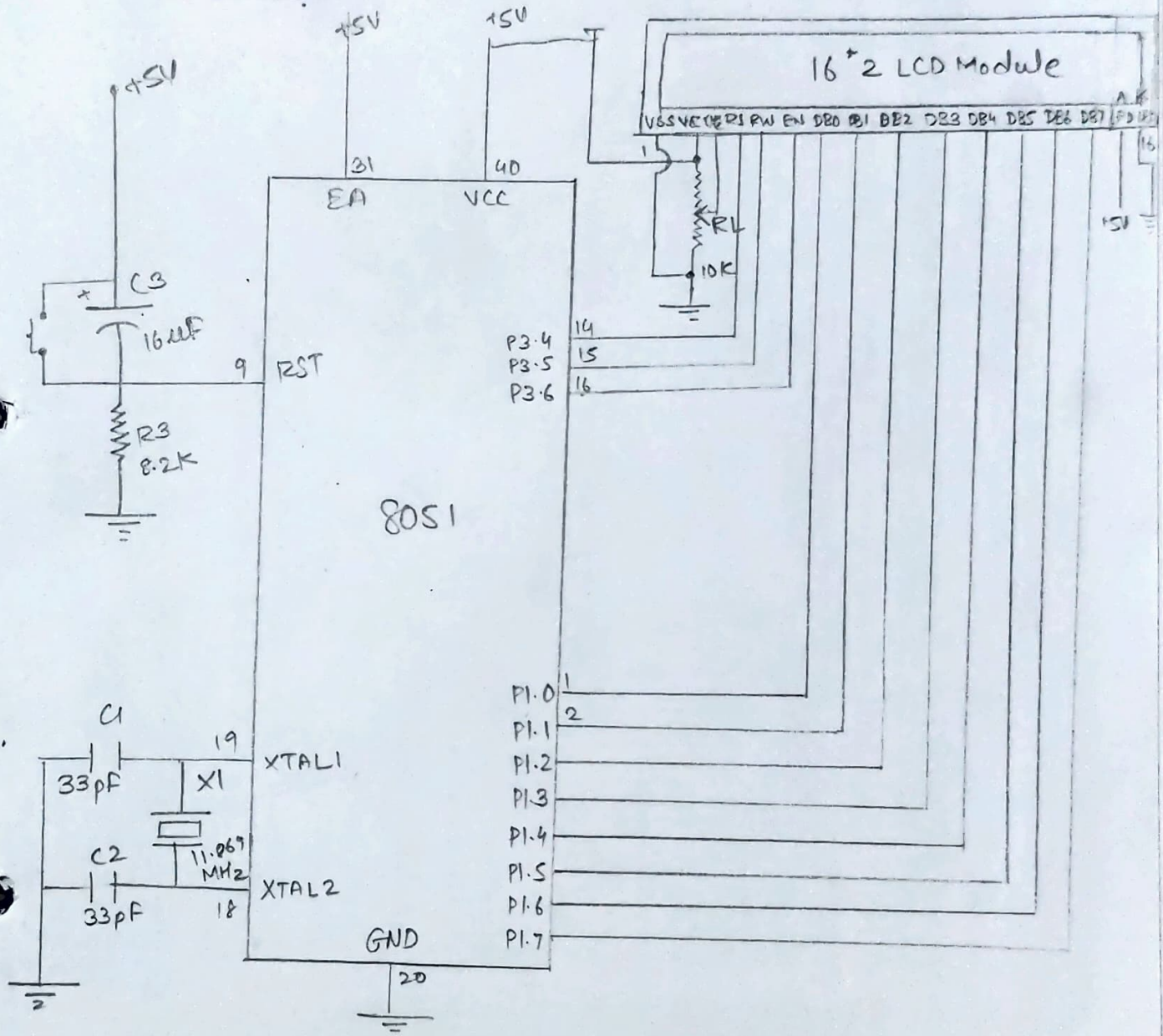


Conclusion:

Thus, the 16x2 LCD was successfully interfaced with 8051 microcontroller. The required message was displayed using embedded C programming & LCD control signal RS, RW & EN.

Interfacing Diagram:

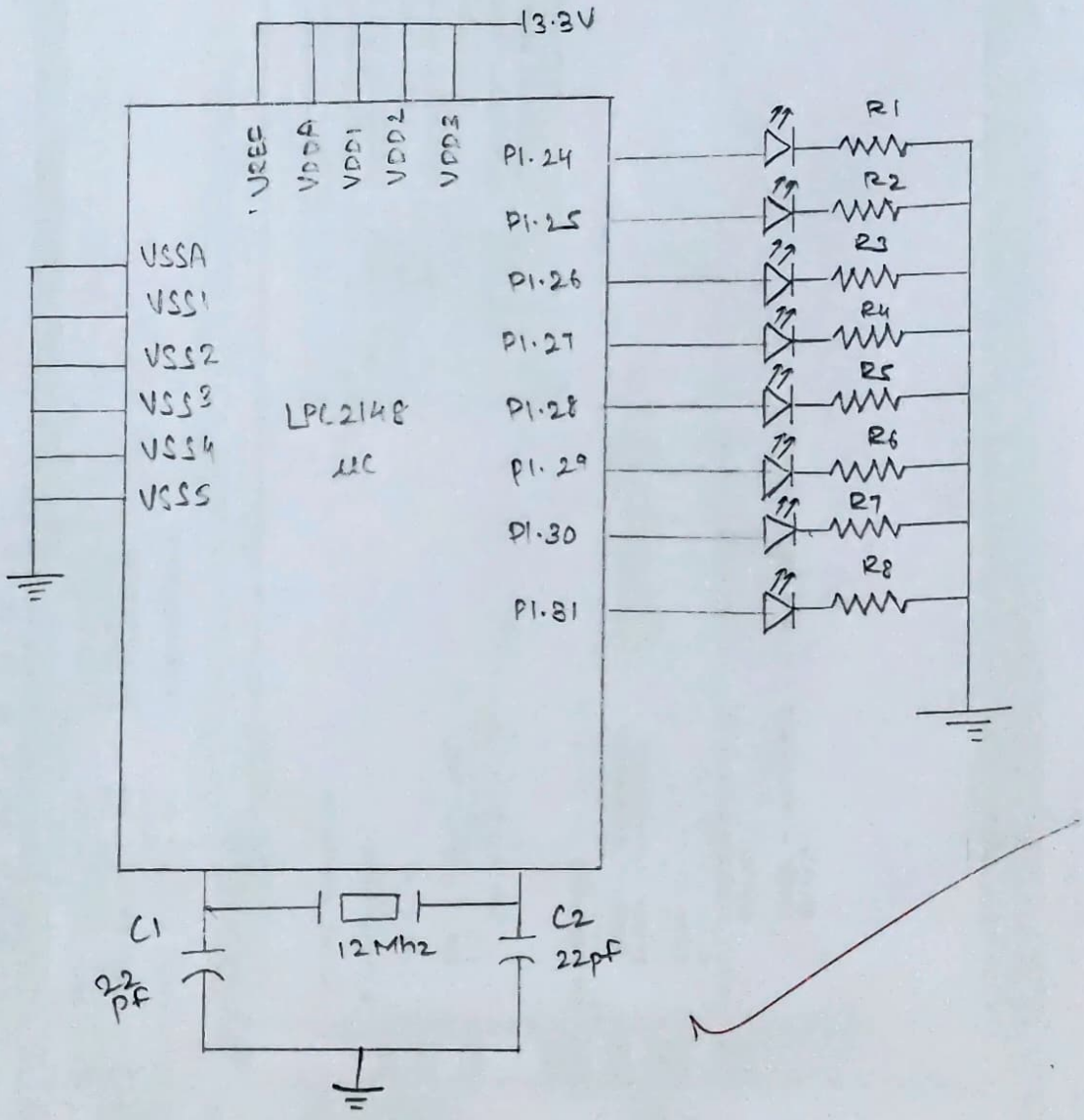Interfacing Diagram (Draw According to your own Program)




Conclusion:

In this practical, we surressfully interfaced LEDs with the LPC2148 ARM7 microcontroller & verified LED bliuking & pattern sequences using GPIO registers in keil uVision.

Interfacing Diagram:

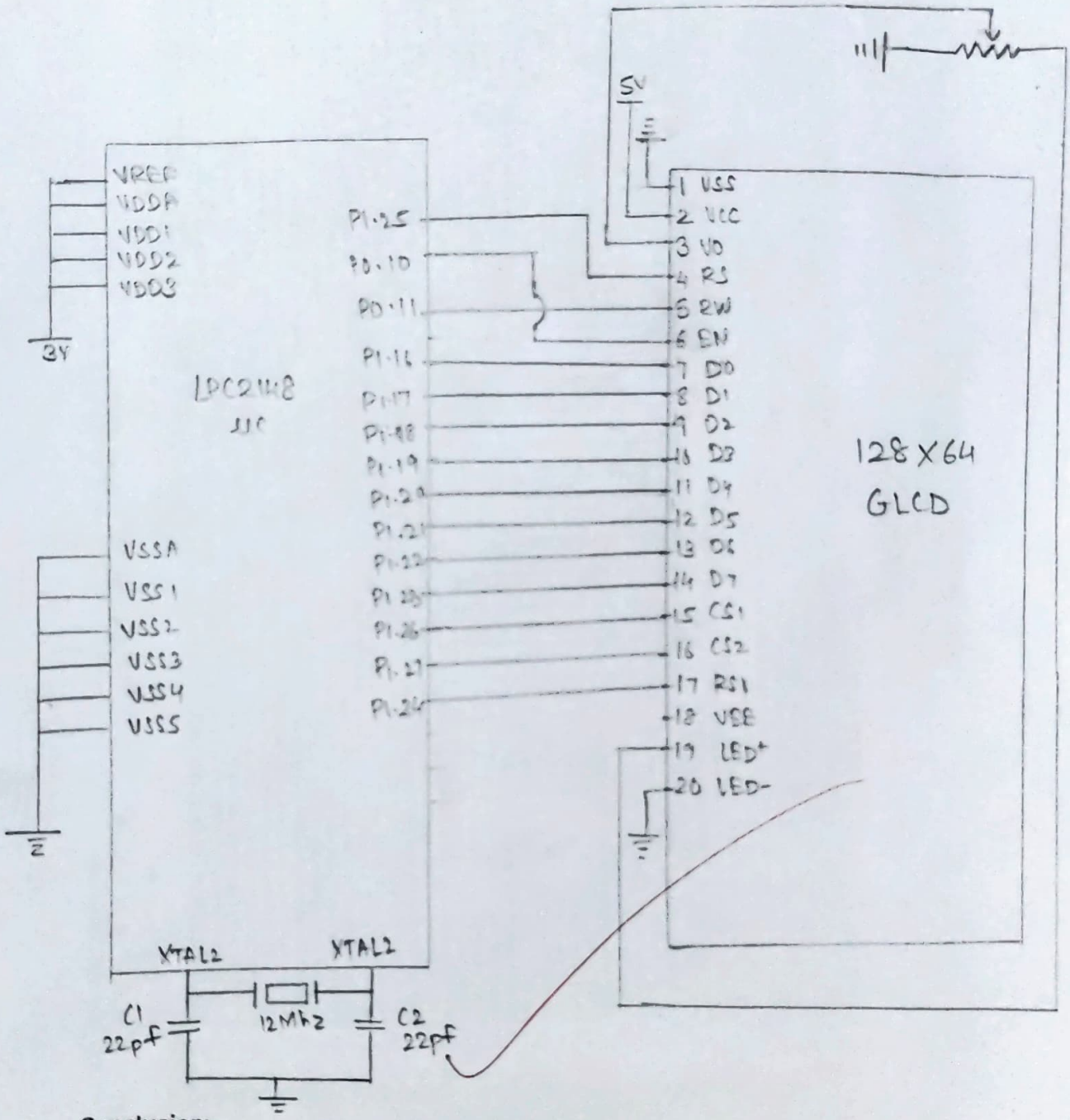Interfacing Diagram (Draw According to your own Program)




Conclusion:

In this practical, we successfully interface a 128x64 Graphical LCD (GLCD) with the LPC2148 ARM7 microcontroller using Keil uVision & Flash Magic & displayed a bitmap image on it.

Interfacing Diagram:

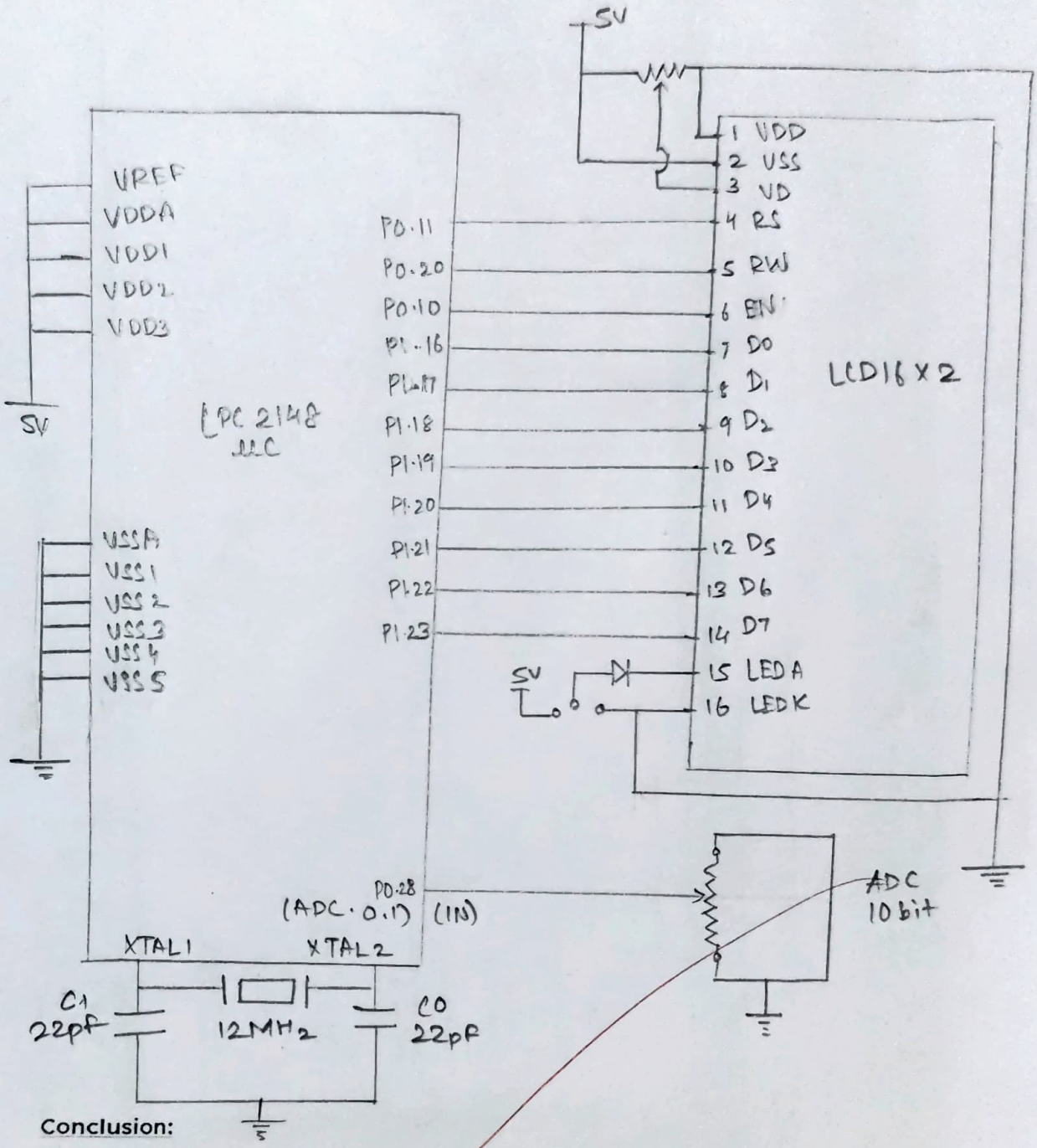Interfacing Diagram (Draw According to your own Program)




Conclusion:

In this practical, we successfully configured & executed Embedded C programs to convert analog input to digital values using the built-in 10-bit ADC of the LPC2148 microcontroller via both polling & interrupt methods.

Interfacing Diagram:

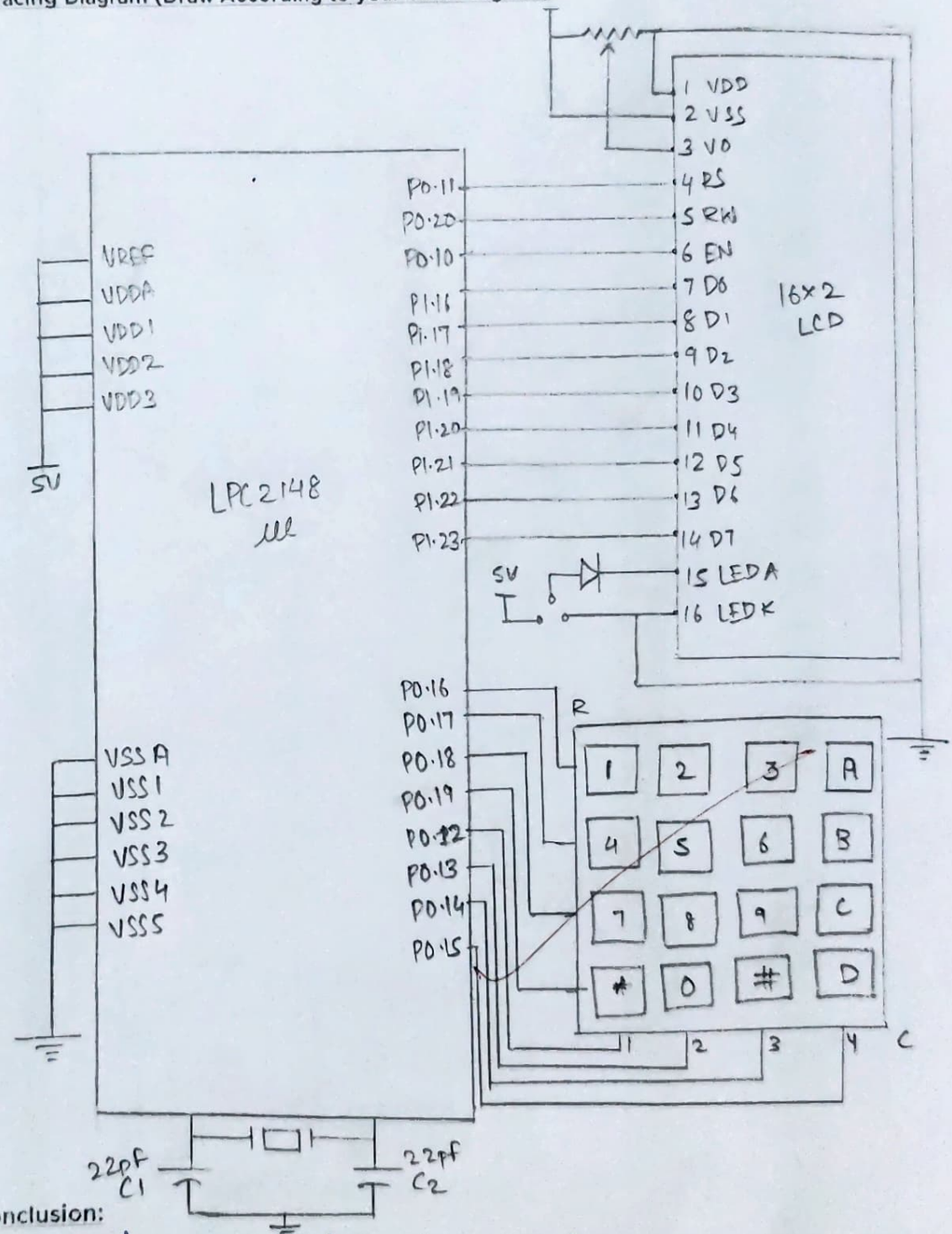Interfacing Diagram (Draw According to your own Program)




Conclusion:

In this practical, we successfully interfaced a 4x4 matrix keypad with the LPC2148 microcontroller using the row-column scanning method & displayed the detected key presses on an LCD.

Interfacing Diagram:

Interfacing Diagram (Draw According to your own Program)

CE = Chip Enable
SCLK = Serial Clock.

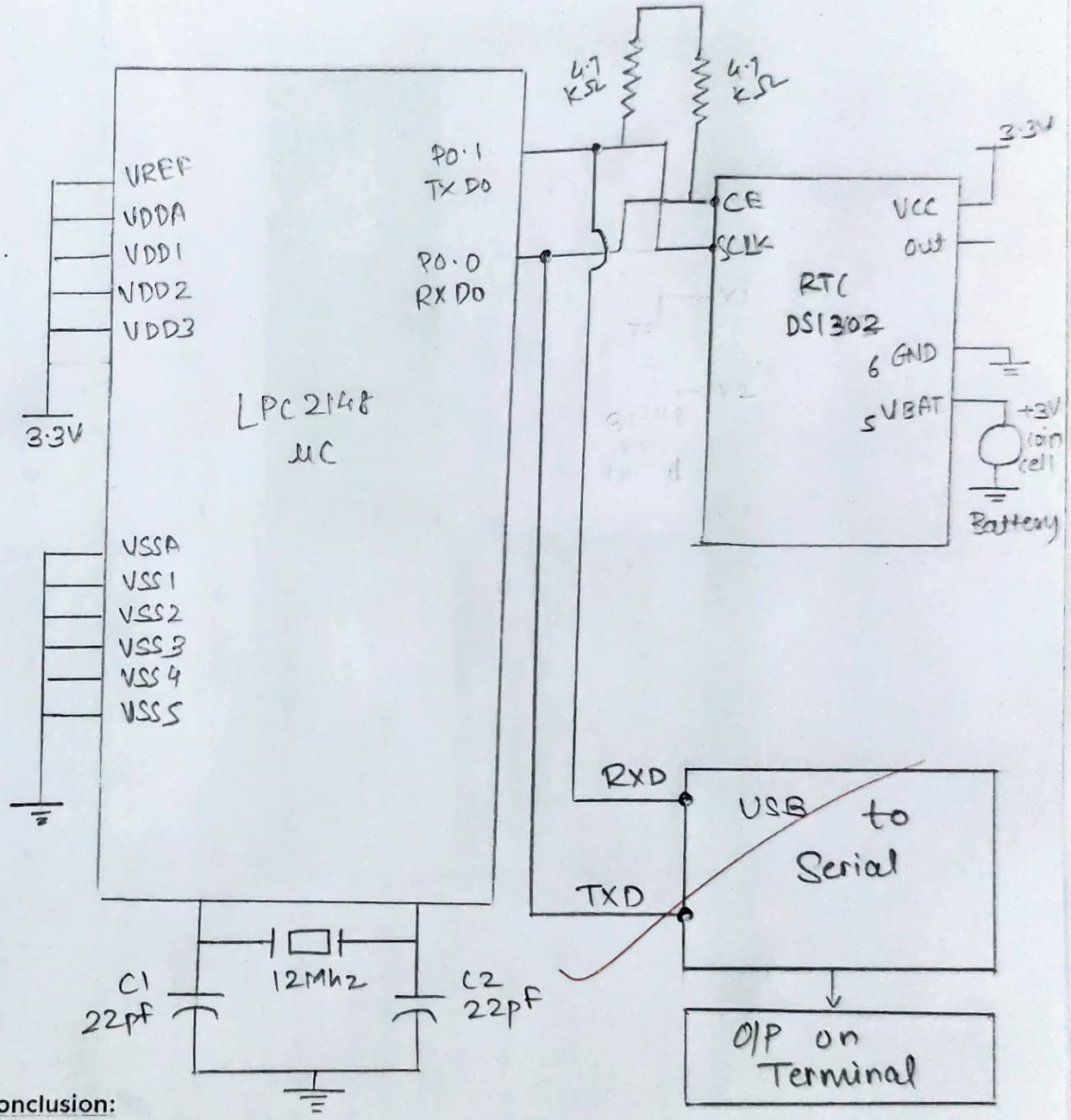


Conclusion:

In this practical, we sucessfully configured & initialized the on-chip RTC of the LPC2148 microcontroller & verified the real-time time and date display via UART serial communication.

Interfacing Diagram:

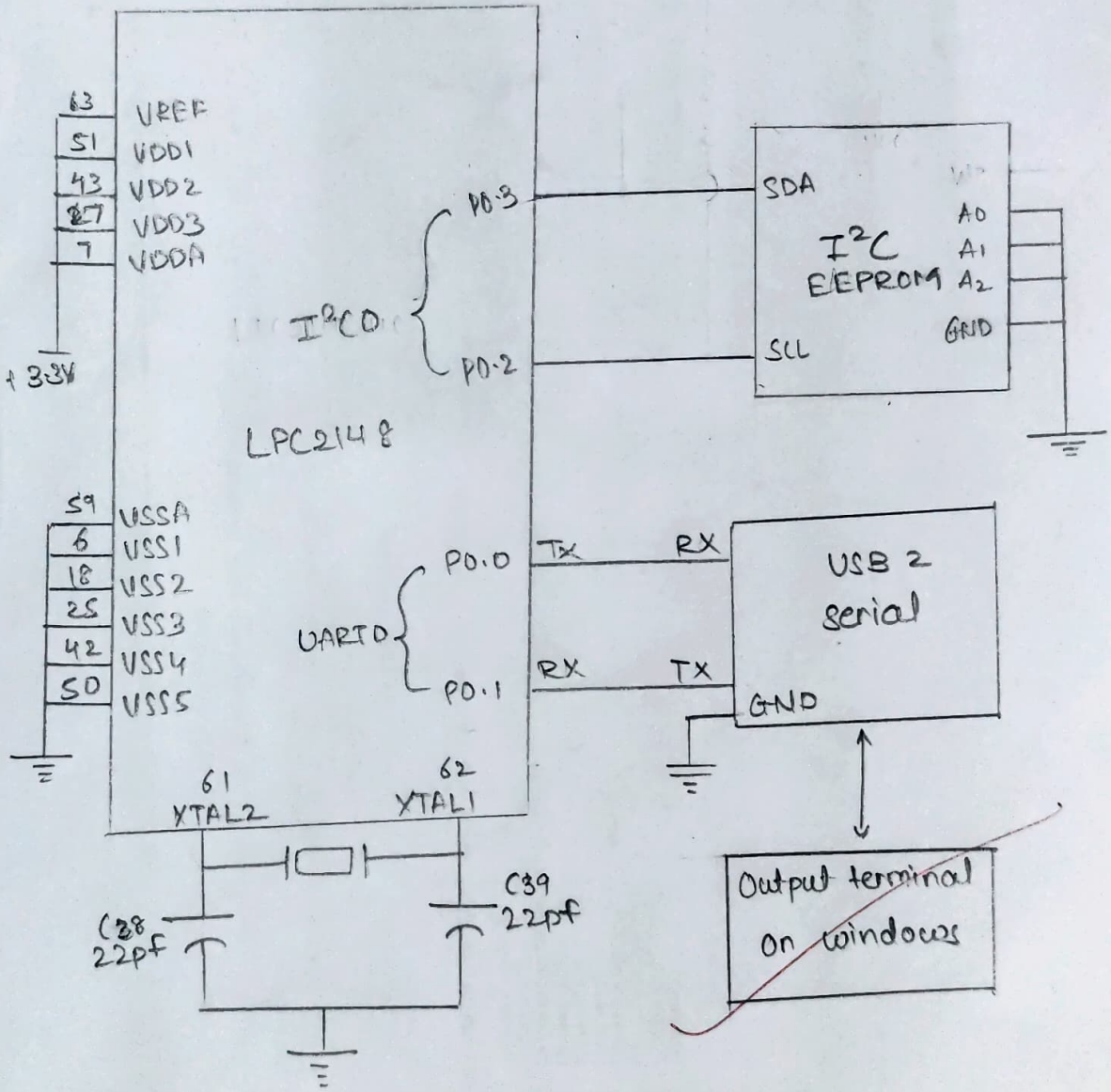Interfacing Diagram (Draw According to your own Program)



Conclusion:

In this practical, we sucessfully interfaced an external EEPROM with the LPC2148 µc using I2C protocol & verified data write & read operations via UART serial communication.